

CSE 260M / ESE 260
Intro. To Digital Logic & Computer Design

Bill Siever
&
Jim Feher

This week


- Thursday:
Studio — Here / Seigle 301
- Hw#5 posted was supposed to be posted by late Friday
 - *Was actually* Monday. Due Sunday at 11:59pm
 - Verilog!

Chapter 5 & 6


Ripple Adder

 - Example: 1111 + 0001
- As a traditional math problem:

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$



Info in circuit

 

- As values in a circuit:

0	0	0	0	<= Carry $i-1$ connected to carry in of i
1	1	1	1	<= "A"
0	0	0	1	<= "B"
0	0	0	0	<= "Sum"

Info in circuit: Initial

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 0 & 0 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{"A"} \\ + & 0 & 0 & 0 & 1 & \leq \text{"B"} \\ \hline 0 & 0 & 0 & 0 & \leq \text{"Sum"} \end{array}$$

Info in circuit: After 1st “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 0 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 1 & 1 & 1 & 0 & \leq \text{“Sum”} \end{array}$$

Info in circuit: After 2nd “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 1 & 1 & 0 & 0 & \leq \text{“Sum”} \end{array}$$

Info in circuit: After 3rd “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 1 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 1 & 0 & 0 & 0 & \leq \text{“Sum”} \end{array}$$

Info in circuit: After 3rd “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 1 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 0 & 0 & 0 & 0 & \leq \text{“Sum”} \end{array}$$

Ripple Adder: Total Time

- N bits: Worst case scenario is ripple through all N
 - If T_c is the propagation delay through the Carry
= $N \cdot T_c$
 - Dictates things like maximum clock cycle for any paths/loops that use addition
 - Lots of things rely on addition!

JLS

Wikipedia Animation

Carry Look-Ahead

- Divide large addition into n -bit blocks
- Within each block, determine if what each column would with a carry-in to the column


- Would it “Generate” a carry? (g_x)

$$\begin{array}{r} ? \leq \text{Carry in} \\ a \leq \text{“A”} \\ + b \leq \text{“B”} \\ \hline s \leq \text{“Sum”} \end{array}$$


- Would it merely “Propagate” the carry? (p_x)

- Can the carry-out be represented in terms of a_x, b_x, cin_x, g_x and p_x ?

Building a Block (of 4)

 


Extend “prediction” to block

 


$$P_{block} = P_3 \cdot P_2 \cdot P_1 \cdot P_0$$

$$G_{block} = G_3 + P_3 \cdot (G_2 + (P_2 \cdot (P_1 \cdot G_0)))$$

Block “Prediction”

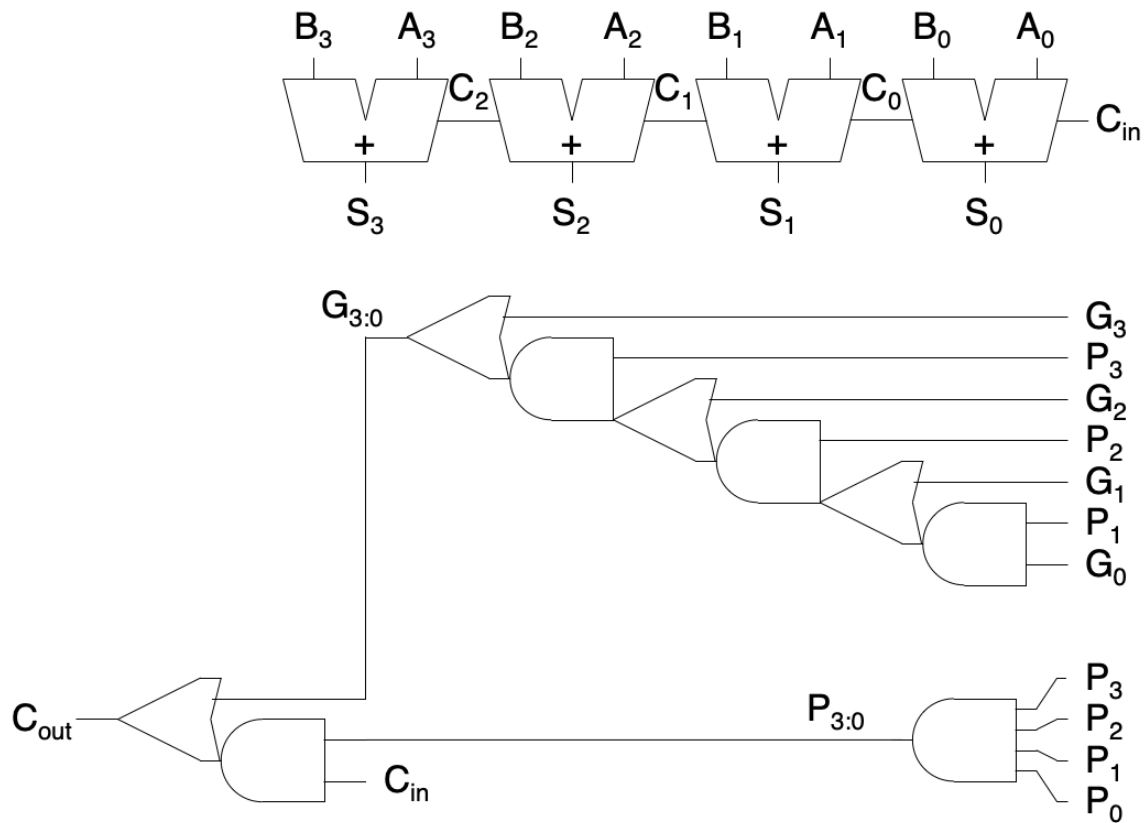

Ripple in 4 block, 16-bit CLA

 


Trade off: Logic vs. Time

- CLA and other tricks (Prefix adder) add logic to reduce time
- Degenerate Case: A look-up table (full sum-of-products equation)
 - How many layers of logic? (Nots, ands, ors)?
 - To estimate complexity, how many rows and output columns are in a table to add two, 8-bit numbers?
 - Approximately how many AND gates?
Approximately how many OR gates?
Estimate the number of inputs that may be needed on OR gates

Subtraction

- The beauty of 2's complement


- $A - B = A + \bar{B} + 1$

 

Subtraction


- The beauty of 2's complement

- $A - B = A + \bar{B} + 1$

 

Comparisons

 - Equality
 - Easy: Are any bits different?
- Equal to zero?
- ?



Comparisons


- Less than (signed): Is $A < B$?
- Leverage Subtraction: $A < B$ is equivalent to $A - B < 0$
 - Subtract and check result
 - General: Is $A - B$ negative?
 - But...large numbers can “overflow”.
Need to consider overflow and signs of A & B

ALU: Arithmetic Logic Unit

- “Heart” of CPU: Does the computation stuff.

- Basic operations

 - Addition
- Subtraction
- Bitwise AND
- Bitwise OR
- Comparison (<)




ALU: Arithmetic Logic Unit

- “Heart” of CPU: Does the computation stuff.

- Basic operations

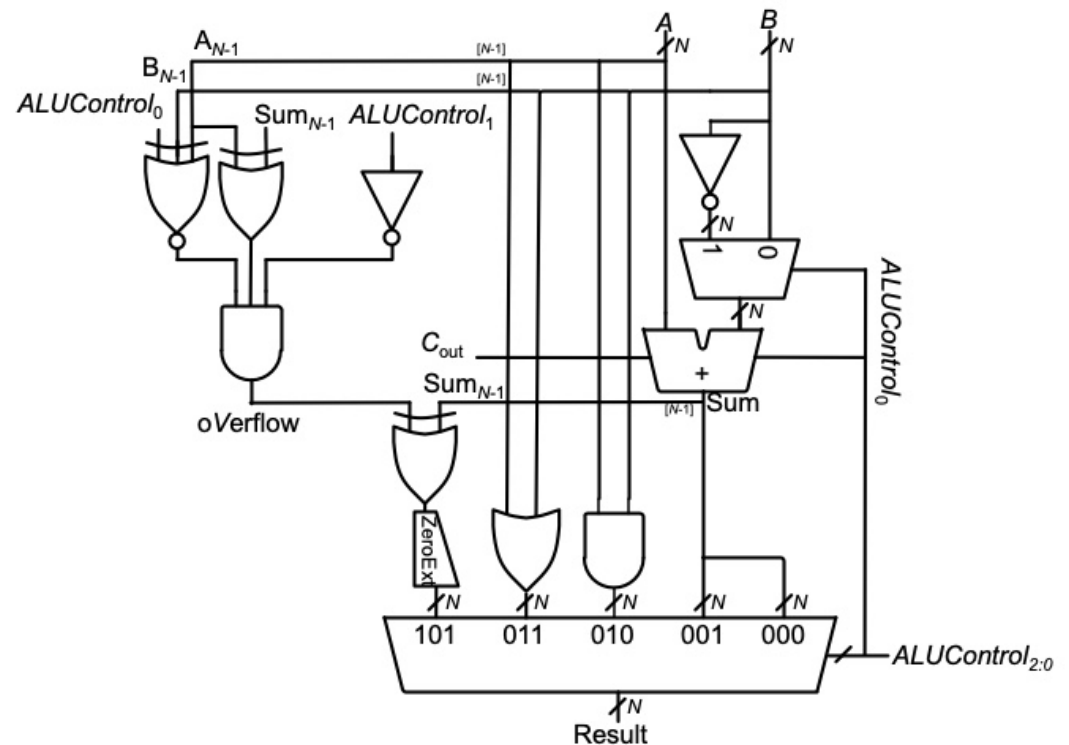- Addition: 000
- Subtraction: 001
- Bitwise AND: 010
- Bitwise OR: 011
- Comparison (<): 101



Memory / Storage

- Common types
 - Static Random Access Memory (SRAM)
 - Dynamic Random Access Memory
 - Read Only Memory (contents can't be easily changed)

Memory / Storage

- General Approach
 - Store in a 2D grid of elements
 - Call each row a “word”
 - Each row has an index to access the content of the entire row
 - Concept: Computer programming
 - An Array (List) is a representation of memory

RAM: SRAM vs. DRAM

SRAM vs. DRAM


- S = “Static”/Unchanging (well, only changing when requested!)
 - Could be build from D Flip Flops (or similar “self-reinforcing” circuits)
- D = Dynamic: Values fade if not refreshed
- RAM: “Random Access”
 - About performance of reading/updating
 - Time take (*propagation delay*) does not depend on index requested

ROM

- Read Only
 - But still “Random Access” performance
- Fixed look-up table. Could be built with combinational logic!
 - Earlier example of “adder” could just be a ROM


Reading Memory

 - M = Word size
- N = “address size”
- How many total bits are stored?




Memory Structure

 - One approach
- Bits are “enabled” to connect to shared output line



ALU Operations

 - Need TWO inputs: need a memory structure that provides two values (I.e. dual output ports)
- The “Register File”
- Also supports writing (updating)



JLS Register File (W/ D Flip Flops)

FPGA

- Field Programmable
- Gate Array
 - Lattice iCE40 UP5k: Architecture Overview
 - RAMs, (Dual and Single Port)
 - Look Up Tables (LUTs): 4 inputs
 - D Flip Flops
 - Lots: ~5,000

Next Time

- Studio